

RESEARCHING PROJECT

“ SOIL PH METER DESIGN ”

[4TH WEEK REPORT]

LECTURER: HEL CHANTHAN
BY: NHIM CHANRENGSEY

2019-2020

OUTLINE

❖ Amplifier(Operational amplifier):

- Inverting Op-Amp
- Non-Inverting Op-Amp
- Summing amplifier
- Differential amplifier
- Op-amp as Integrator
- Op-amp as Differentiator

❖ Missing and Difficulty


AMPLIFIER

- ❖ Why do we have to built filter?
 - Because we need to increase or decrease input.(Gain >1, Gain<1)
- ❖ How can filter help in our circuit?
 - Because of our sensor generate small voltage input, so micro-controller is hard to analyze result to show output.
- ❖ How can we apply filter to our circuit?
 - We need read sensor's datasheet for output and micro-controller's ADC input that can generate to output.
- ❖ How can we built filter for our sensor?
 - We have to know Gain and bandwidth for our sensor to micro-controller then we can built Amplifier for it.
- ✓ We use Operational Amplifier (Op-Amp) for built our Amplifier.


OPERATIONAL AMPLIFIER

Circuit symbol of the operational amplifier:

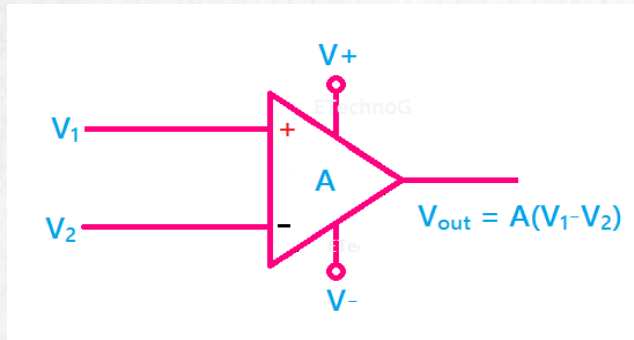
- 2 input and 1 output
- Most of the operational amplifiers consist of two power supplies(positive and negative power supply)




$$V_{out} = A(V_1 - V_2)$$

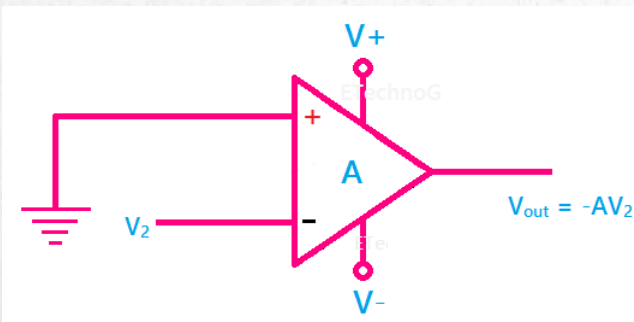


$$V_{out} = A.V_2$$

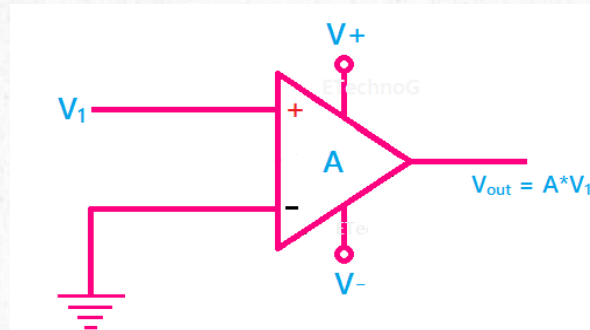

$$V_{out} = A.V_1$$

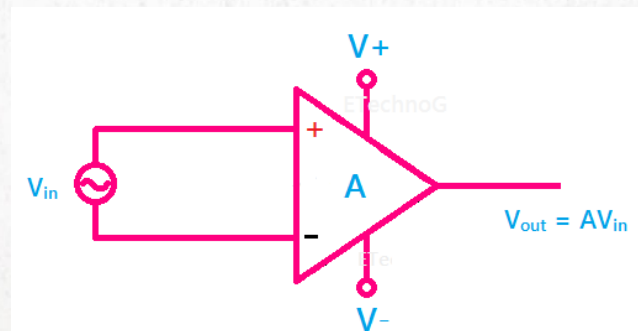
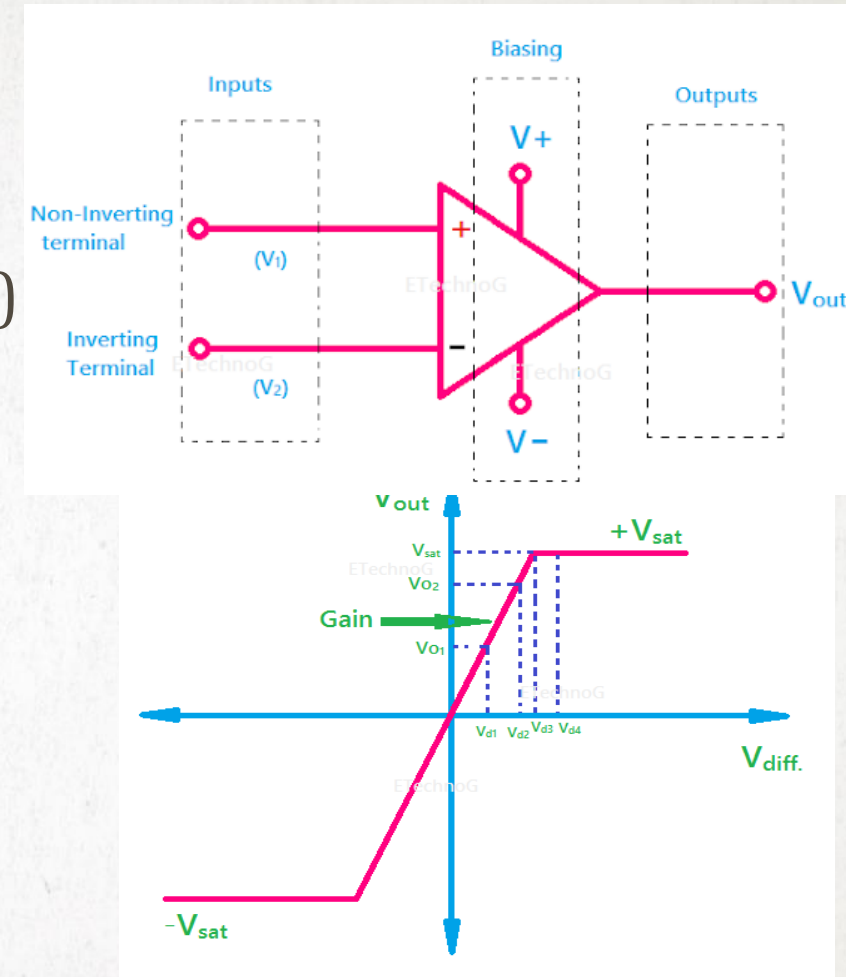
$$V_{out} = A.V_{in} \text{ (high gain)}$$



Value of gain is used in range of 10^5 to 10^6 . Example $V_{in} = 1\text{mV}$ so $V_{out} = 1\text{m} \times 10^5 = 100\text{V}$.


OPERATIONAL AMPLIFIER

Ideal of the operational amplifier Characteristics:


- Input Impendent: $R_{in} = \infty (\text{M}\Omega)$
- Output Impendent: $R_{out} = 0 (\Omega)$
- Open-loop Gain ($A = \infty$)
- $V_{out} = 0$ when $V_{in} = 0$;
- Infinite Bandwidth and Slew Rate
- Infinite CMRR (Common mode rejection ratio)

OP-AMP 741 Specification

Parameters	Values
Input Impendent	2M Ω
Output Impendent	75 Ω
Open-loop Gain	10 ⁵
Offset Voltage	1mV
Slew Rate	0.5 V/ μ s
CMRR	70 – 90 dB

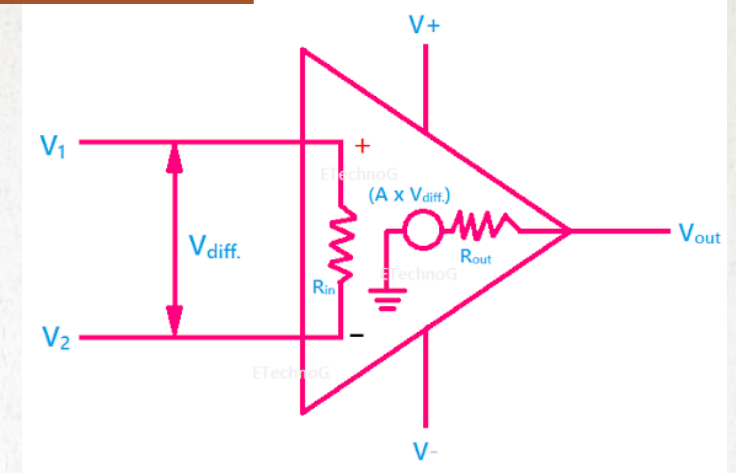

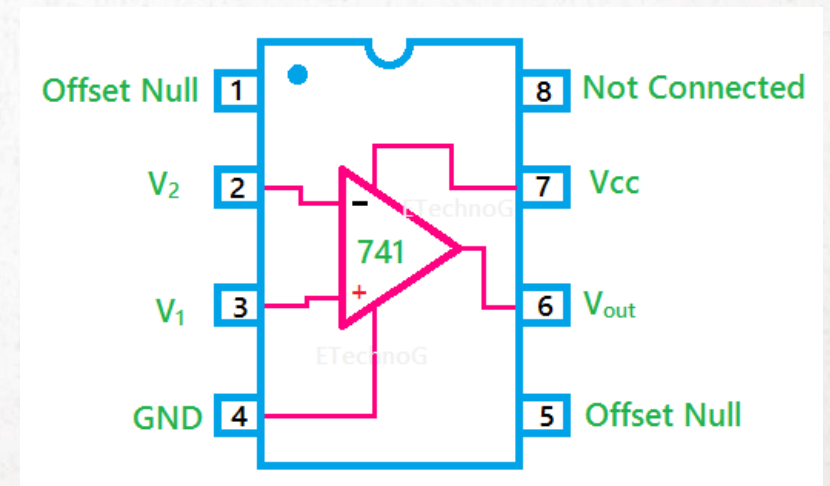$R_{in} = \infty$ and $R_{out} = 0 \Rightarrow BW = (0 - \infty) = \infty$
 $\Rightarrow A = \infty \Rightarrow V_{out} = 0$;



INVERTING OP-AMP

By KCL: $I_{in} = I_f$

For $I_{in} = \frac{V_{in} - V_x}{R_{in}}$ and $I_f = \frac{V_x - V_{out}}{R_f}$; $V_x = 0$



$$\Rightarrow \frac{V_{in}}{R_{in}} = -\frac{V_{out}}{R_f} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

So $Gain(A_v) = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$

Thus $V_{out} = -A_v \cdot V_{in}$

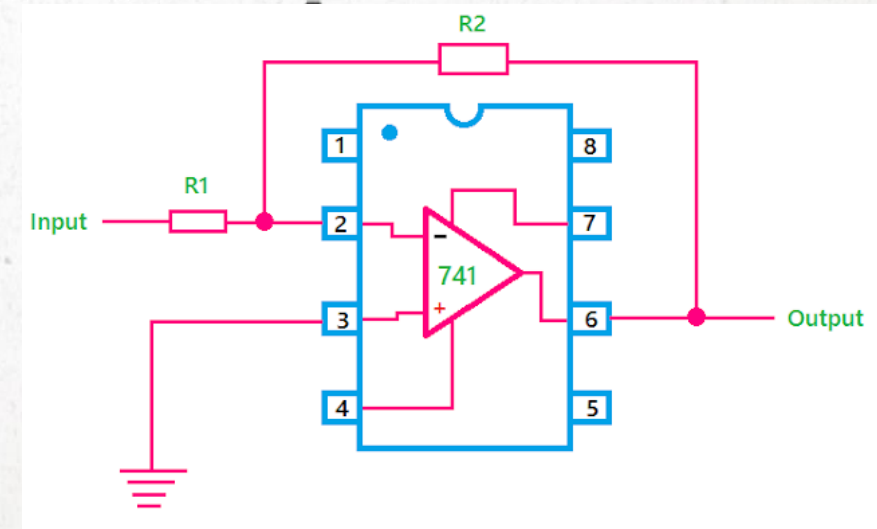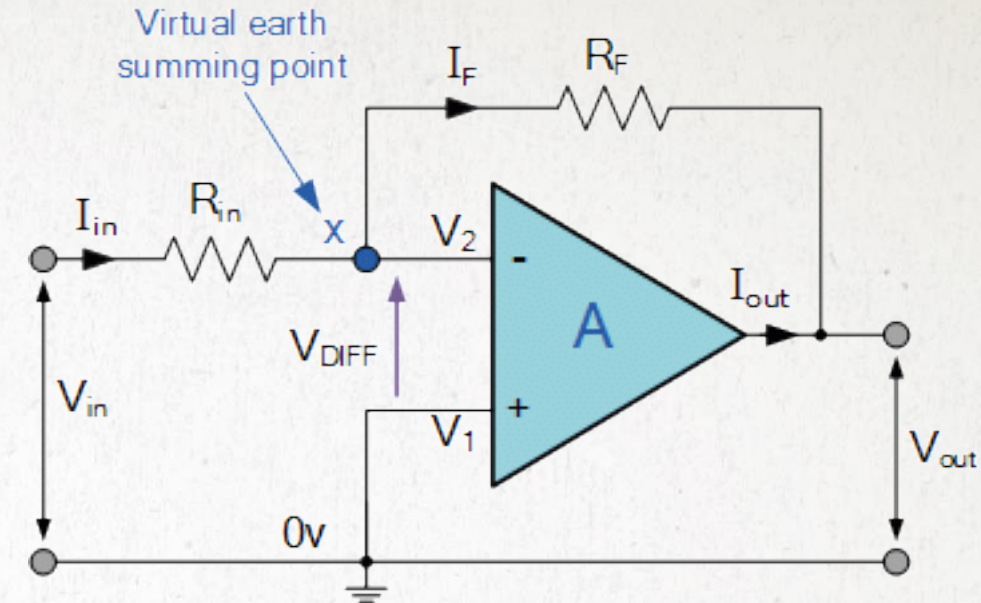Example: $R_{in} = R_f = 1k$

And $V_{in} = 2V \Rightarrow A_v = -1 \Rightarrow V_{out} = -2V$



NON-INVERTING OP-AMP

By $V^+ = V^- \Rightarrow V_1 = V_{in}$



For $V_1 = \frac{R_2}{R_2 + R_f} \times V_{out}$ and $V_{out} = \frac{R_2 + R_f}{R_2} \times V_{in}$

So $Gain(A_v) = \frac{V_{out}}{V_1} = \frac{R_2 + R_f}{R_2} = 1 + \frac{R_f}{R_{in}}$

Thus $V_{out} = A_v \cdot V_{in} = \left(1 + \frac{R_f}{R_2}\right) \cdot V_{in}$

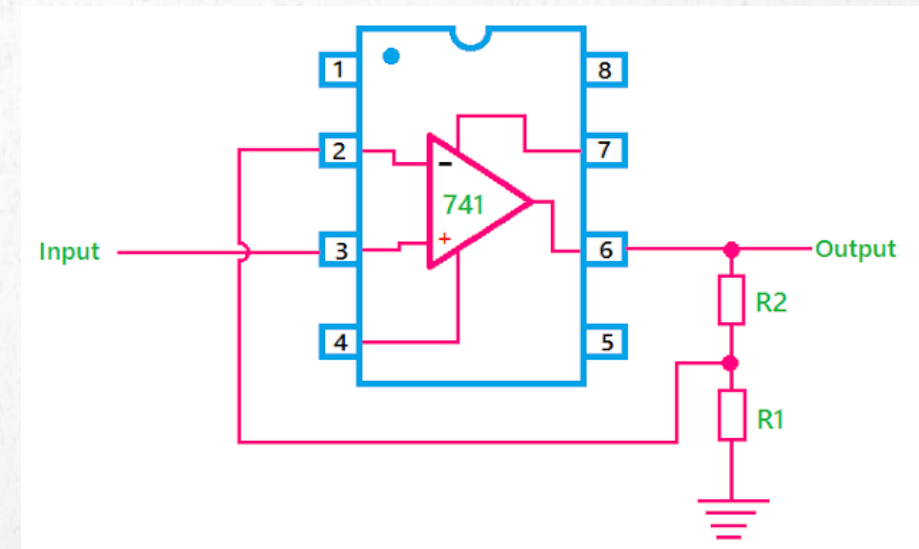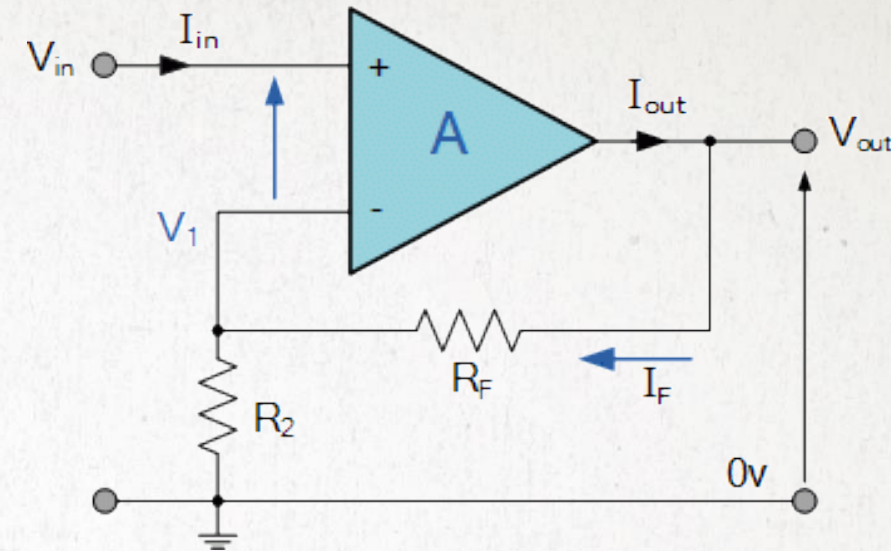Example: $R_2 = R_f = 1k$

And $V_{in} = 2V \Rightarrow A_v = 2 \Rightarrow V_{out} = 4V$




SUMMING AMPLIFIER(INVERTING OP-AMP)

By KCL: $I_F = I_1 + I_2 + I_3 = - \left[\frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}} \right]$

$$\frac{V_{out}}{R_f} = I_f$$

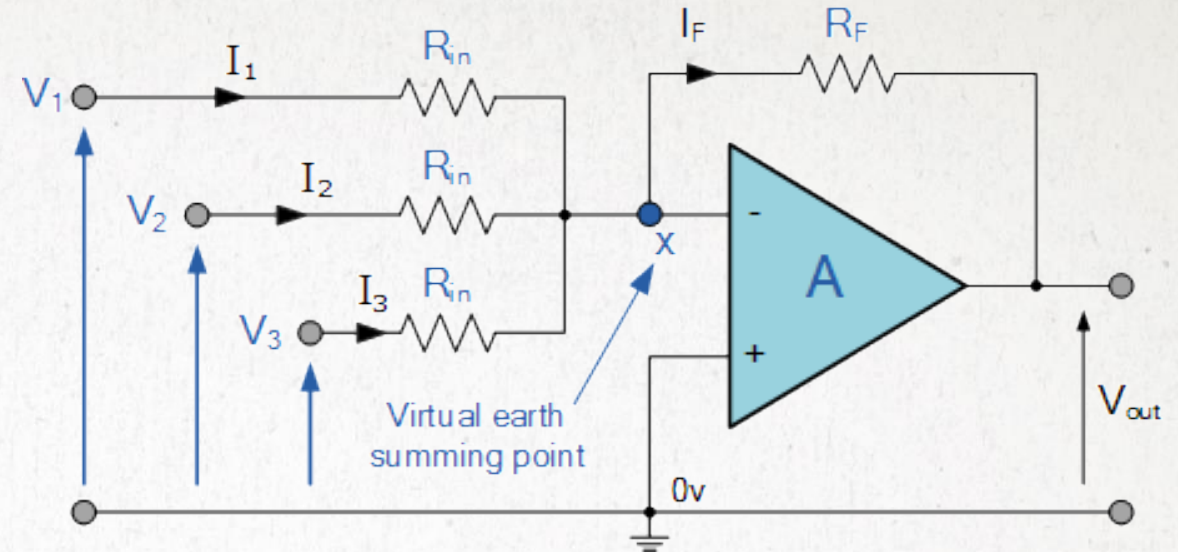then, $-V_{out} = \left[\frac{R_F}{R_{in}} V_1 + \frac{R_F}{R_{in}} V_2 + \frac{R_F}{R_{in}} V_3 \right]$



- Case: $R_1 = R_2 = R_3 = R_F \Rightarrow R_{in} = R_F$ Thus $V_{out} = - (V_1 + V_2 + V_3)$
- Case: $R_1 \neq R_2 \neq R_3 \Rightarrow \frac{R_F}{R_1} \neq \frac{R_F}{R_2} \neq \frac{R_F}{R_3}$ Thus $V_{out} = -(A V_1 + B V_2 + C V_3)$
- Case: $R_1 = R_2 = R_3 = R_{in} \neq R_F$ Thus $V_{out} = - \frac{R_F}{R_{in}} (V_1 + V_2 + V_3)$

SUMMING AMPLIFIER(NON-INVERTING OP-AMP)

$$I_{R1} + I_{R2} = 0 \quad (\text{KCL})$$

$$\frac{V_1 - V_+}{R_1} = \frac{V_2 - V_+}{R_2} = 0$$

$$\therefore \left(\frac{V_1}{R_1} - \frac{V_+}{R_1} \right) + \left(\frac{V_2}{R_2} - \frac{V_+}{R_2} \right) = 0$$

If we make the two input resistances equal in value, then $R_1 = R_2 = R$.

$$V_+ = \frac{\frac{V_1}{R} + \frac{V_2}{R}}{\frac{1}{R} + \frac{1}{R}} = \frac{V_1 + V_2}{2}$$


$$\text{Thus } V_+ = \frac{V_1 + V_2}{2}$$

The standard equation for the voltage gain of a non-inverting summing amplifier circuit is given as:

$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{V_{OUT}}{V_+} = 1 + \frac{R_A}{R_B}$$

$$\therefore V_{OUT} = \left[1 + \frac{R_A}{R_B} \right] V_+$$
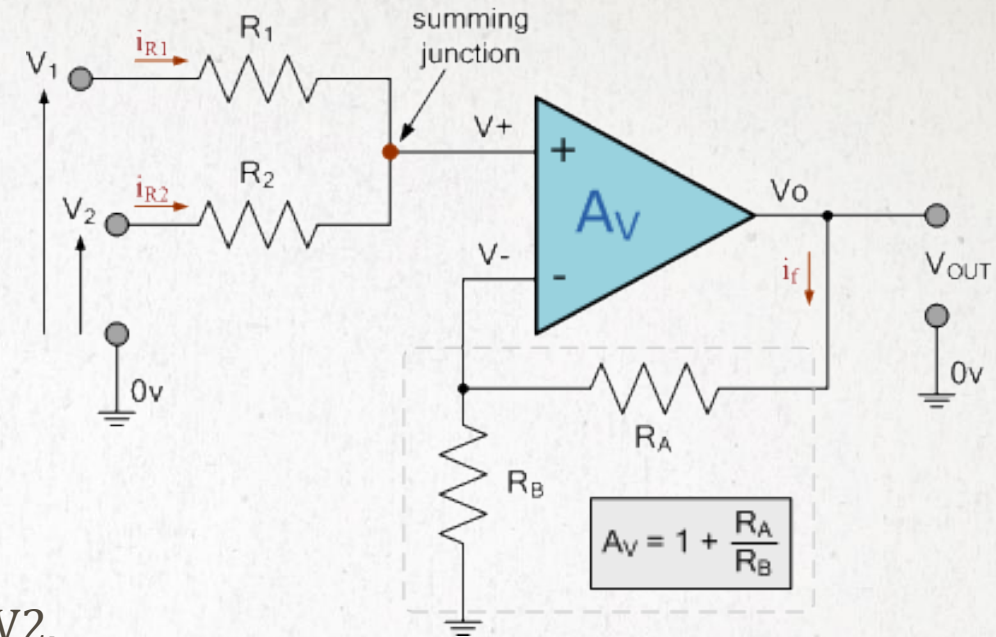
$$\text{Thus: } V_{OUT} = \left[1 + \frac{R_A}{R_B} \right] \frac{V_1 + V_2}{2}$$



❖ Case $R_A = R_B$

Thus $V_{out} = V_1 + V_2$.

❖ Case $R_1 \neq R_2$ and $R_A \neq R_B$:

$$V_{out} = \left(1 + \frac{R_A}{R_B} \right) \left(\frac{R_2}{R_1 + R_2} \times V_1 + \frac{R_1}{R_1 + R_2} \times V_2 \right)$$

DIFFICULTY AND MISSING

❖ Difficulty :

- Many resource to read and learn
- Don't have enough time.

❖ Missing:

- Lately work

PLANNING FOR 1ST MONTH

Week	Monday	Tuesday	Wednesday	Thursday	Friday	Goal
1 st Week	Research	Meeting	Learn Amplifier	Presentation	Learn Filter	Learn Filter
2 nd Week	REST DAYS					
3 rd Week	Learn Filter	Learn Filter	Learn Filter	Learn Filter	Learn Filter	Learn Filter
4 th Week	Learn Amplifier	Learn Amp Meeting	Learn Amplifier	Presentation Learn Amp	Learn Amplifier	Learn Amplifier

Start : 10/08/2020

PLANNING FOR 2ND MONTH

Week	Monday	Tuesday	Wednesday	Thursday	Friday	Goal
5 th Week	Build Filter pH & LCD	Meeting Build Filter	Filter Build filter	Presentation Build Amp	Build Amplifier	Design Amplifier
6 th Week	Build Amplifier	Meeting Learn stm32	Learn STM32 Test LCD/pH	Presentation Write Code	Write Code STM32	Start STM32
7 th Week	Write Code STM32	Meeting Write Code	Write Code STM32	Presentation Write code	Finish STM32 Code	Finish STM32 Code
8 th Week	Draw case for hardware	Meeting Draw case	Draw case for hardware	Presentation Draw case	Print 3D case	Build case Finish Job

Start : **06/09/2020**



**THANK
YOU**